

## ANNOUNCEMENTS

What is  $(1 + i)^2/(1 - i)$ ?

- A.  $e^{i\pi/4}$
- B.  $\sqrt{2}e^{i\pi/4}$
- C.  $e^{i3\pi/4}$
- D.  $\sqrt{2}e^{i3\pi/4}$
- E. Something else!

- Project problems are graded
  - Sync your repositories to receive feedback
  - Responding to your feedback is a big part of the next project problem
- Quiz 3 (next Friday 2/17) - RLC circuits
  - Solve a circuit problem using the phasor method
  - Discuss limits on the response and how it might act as a filter

For the RL circuit with driving voltage of  $V(t) = V_0 \cos(\omega t)$ , we found a solution for the current as a function of time, with  $I = 0$  at  $t = 0$ ,

$$I(t) = a \cos(\omega t + \phi) - a \cos(\phi)e^{-Rt/L}$$

where  $a = \frac{V_0}{\sqrt{R^2 + L^2 \omega^2}}$  and  $\phi = \tan^{-1}(-L\omega/R)$ . What happens to the current when  $\omega \rightarrow \infty$ ?

- A. Current is essentially zero, for all time
- B. Current dies off completely, eventually goes to zero
- C. Eventually, current is constant,  $V_0/R$
- D. It depends
- E. ???


For the RL circuit with driving voltage of  $V(t) = V_0 \cos(\omega t)$ , we found a solution for the current as a function of time, with  $I = 0$  at  $t = 0$ ,

$$I(t) = a \cos(\omega t + \phi) - a \cos(\phi)e^{-Rt/L}$$

where  $a = \frac{V_0}{\sqrt{R^2 + L^2 \omega^2}}$  and  $\phi = \tan^{-1}(-L\omega/R)$ . What happens to the current when  $\omega \rightarrow \infty$ ?

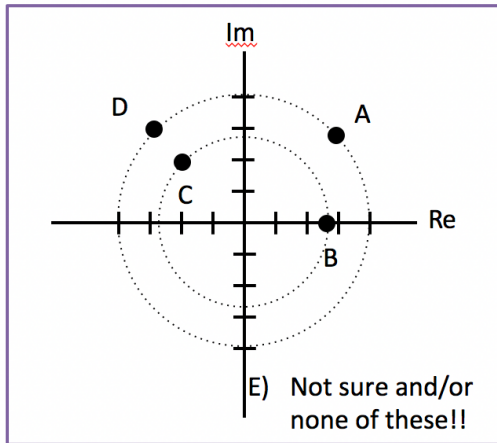- A. Current is essentially zero, for all time
- B. Current dies off completely, eventually goes to zero
- C. Eventually, current is constant,  $V_0/R$
- D. It depends
- E. ???

Which point below best represents  $4e^{i3\pi/4}$  on the complex plane?



What is the total impedance of this circuit,  $Z_{total}$ ?

- A.  $R + i\left(\omega L + \frac{1}{\omega C}\right)$
- B.  $R + i\left(\omega L - \frac{1}{\omega C}\right)$
- C.  $\frac{1}{R} + \frac{1}{i\omega L} + i\omega C$
- D.  $\frac{1}{\frac{1}{R} + \frac{1}{i\omega L} + i\omega C}$
- E. None of these

